

Protected qubits using

Josephson junctions and other
superconducting elements.

Goal : all-electric protected*
qubits

(Qubits are not elementary devices)

Sub-goal : find a set of basic
elements for quantum
electric circuits

* Protected =

All unwanted interactions are
exponentially suppressed.

"Simple" elements:

Capacitor:



Standard

Josephson junction:



Inductor:



Usually implemented
as a chain of
Josephson junctions


$$J \gg \frac{e^2}{C}$$

$$(L_{\text{eff}} = N \left(\frac{\hbar}{2e} \right)^2 J^{-1})$$

Switch:



(Haviland et al)
2000

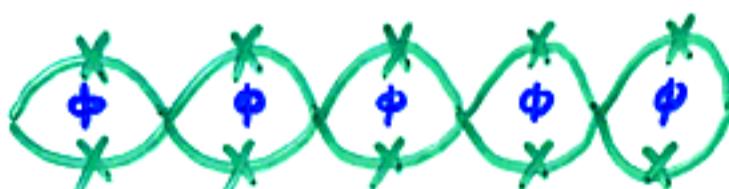

$$\phi \approx \pi$$



(In dimensional
units, $\phi \approx \Phi_0 / 2$)

transition to
an insulating
state

More exotic



elements :

1) $0-\pi$ - contact

(Douçot, Vidal 2002
Ioffe, Feigelman 2002)

$$E = -J_1 \cos(2\varphi) - J_2 g(\varphi)$$


$J_2 \ll J_1$, error term

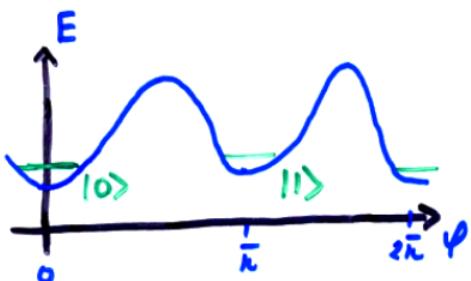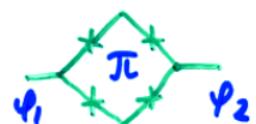

$$\delta E = E_1 - E_0 = 2J_2$$

May depend on the environment \Rightarrow decoherence

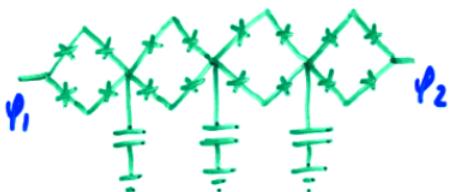2) Protection (stabilization) $\delta E_{\text{eff}} \rightarrow 0$



$$|0_L\rangle = |0000\rangle + |1100\rangle + \dots$$

(even number of 1s)

$$|1_L\rangle = |1000\rangle + |0100\rangle + \dots$$

(odd number of 1s)

$$J_{1,\text{eff}} \sim \frac{1}{N}$$

$$\delta E_{\text{eff}} \sim \left(\frac{J_2}{t}\right)^{N-1}$$

tunneling amplitude

It seems that quantum protection requires a many-body system because a protected state is similar to a quantum code.

Not quite true : One can use a single continuous degree of freedom for quantum encoding (Gottesman
Kitaev
Preskill 2000)

Main conceptual result of the present work :

A sufficiently large superconducting inductor provides room for quantum encoding.


(Of course, Josephson junctions are also needed)

5

Conventions : $\hbar = 1$, $2e = 1$.

Resistance unit : $\frac{\hbar}{(2e)^2} \approx 1 \text{ k}\Omega$

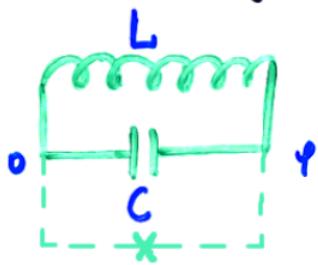In this units, the quantum resistance $R_q = \frac{\hbar}{(2e)^2} \approx 6 \text{ k}\Omega$, is simply 2π .



$$H = \frac{\Psi^2}{2L} + \frac{1}{2C} \underbrace{\left(i \frac{\partial}{\partial \Psi} \right)^2}_{q \text{ (charge operator)}}$$

$$\langle \Psi^2 \rangle = \frac{1}{2} \sqrt{\frac{L}{C}} \quad (\text{characteristic impedance})$$

"Superinductor": $\langle \Psi^2 \rangle$ is large

$$\langle \cos \Psi \rangle = e^{-\frac{\langle \Psi^2 \rangle}{2}} = \exp \left(-\frac{1}{4} \sqrt{\frac{L}{C}} \right)$$

$\sqrt{\frac{L}{C}} \gg 4$ ($4 \text{ k}\Omega$ in the usual units)
in units of $\frac{\hbar}{(2e)^2}$

How to make a superinductor?

1) Coil of n loops: $\sqrt{\frac{L}{C_{\text{geom}}}} \sim R_{\text{vac}} \sqrt{\frac{\mu}{\epsilon}} n$

$$R_{\text{vac}} = \frac{4\pi L}{137} \quad \left(\frac{4n}{c} \approx 377 \Omega \right)$$

Too many loops are needed

2) ~~$\frac{*}{j_c} \frac{*}{j_c} \frac{*}{j_c} \dots$~~ $L = \frac{N}{j}$

$\sqrt{\frac{L}{C_{\text{chain}}}} = \frac{N}{\sqrt{j_c}} \gg 4$, but $\sqrt{j_c} \gg 1$ is necessary to prevent phase slips.

Too many junctions ...

3) Kinetic inductance

d [Some thickness, e.g., 10 nm]
l

$$L \sim \frac{R \cdot l}{\pi d} = \frac{l}{d} \frac{R_\square}{\pi \Delta}$$

Normal state resistance

(Amorphous film)

(Assuming that quantum fluctuations are not too strong)

12

For kinetic inductors, $C_{\text{geom.}}$ is not a limiting factor because usually $\frac{1}{\sqrt{LC_{\text{geom}}}} > \Delta$.

$$\langle \varphi^2 \rangle \sim R = \frac{l}{d} R_\square \quad \text{It is possible that } R_\square \sim 4 \text{ k}\Omega$$


Superinductor requirements:

$$1) \frac{l}{d} \gg \frac{4}{R_\square}$$

$$2) \frac{z}{d} \ll \frac{4}{R_\square} \text{ to prevent phase slips}$$

$\Rightarrow z \sim 30 \text{ \AA}$ in MoGe

Typical application:

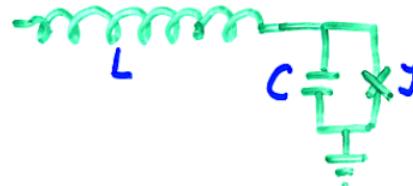

$$\mu = \sqrt{\gamma C} \sim 1$$

(intermediate quantum regime)

$$\text{For Al-Al}_2\text{O}_3 \text{ junctions } \omega_p = \sqrt{\frac{\gamma}{C}} \sim 20 \text{ GHz}$$


$$\gamma \sim C^{-1} \sim \omega_p \Rightarrow C \sim 5 \cdot 10^{-15} \text{ F}$$

$\sim 1 \text{ K}$

in the junction

The geometric capacitance is small if $l < 10 \mu\text{m}$


Adiabatic switch

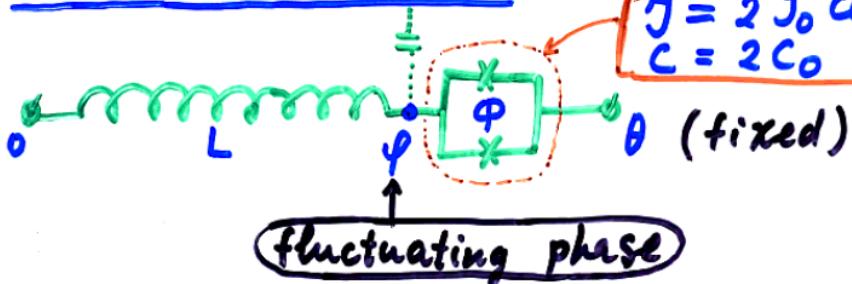

Superconducting current $I(\theta) = \frac{\partial E}{\partial \theta}$

I_{\max} change as a function of γ
by many orders of magnitude
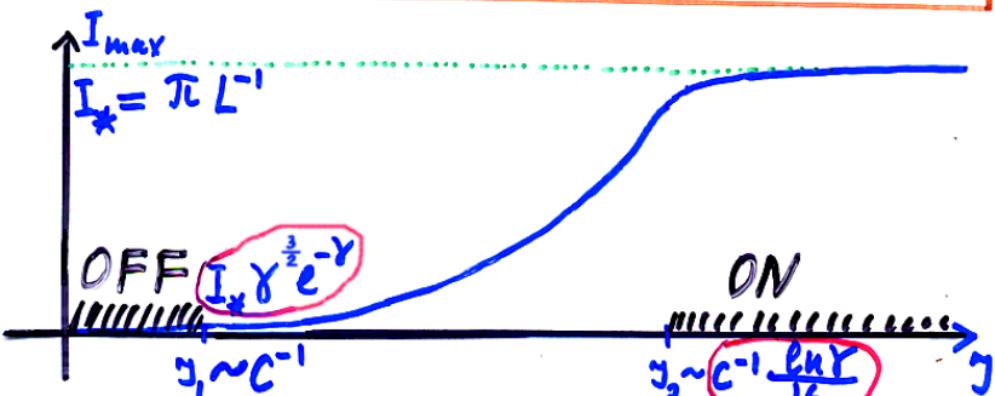
$$H = \frac{\Phi^2}{2L} - \gamma \cos(\phi - \theta) + \frac{1}{2C} \left(i \frac{\partial}{\partial \phi} - n_g \right)^2$$




$$\gamma = \frac{1}{4} \sqrt{\frac{L}{C}}$$

phase slips suppressed


$$U(\varphi) = \frac{\varphi^2}{2L} - J \cos(\varphi - \theta)$$

$\psi(\varphi)$

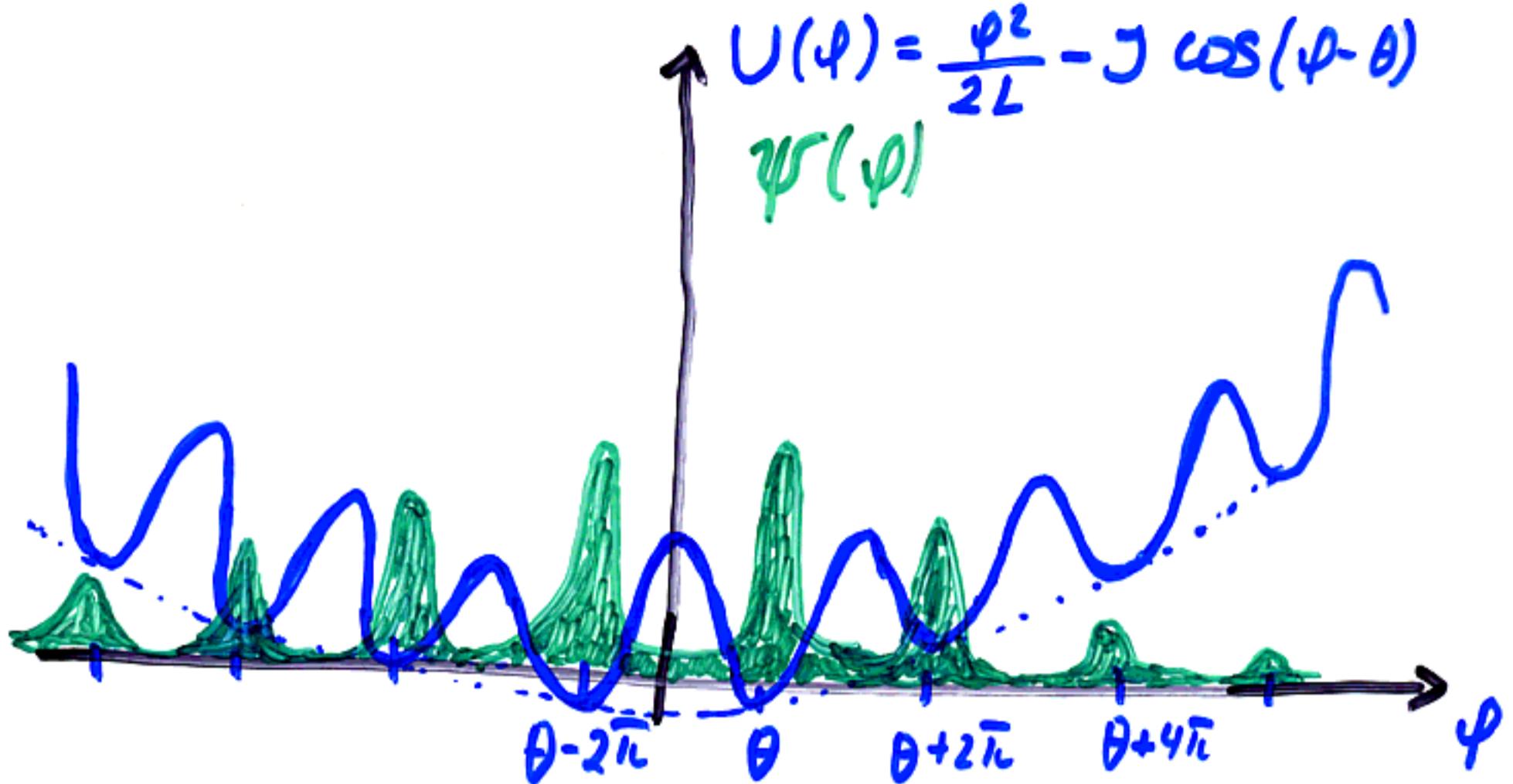

switch OFF

$\psi(\varphi)$

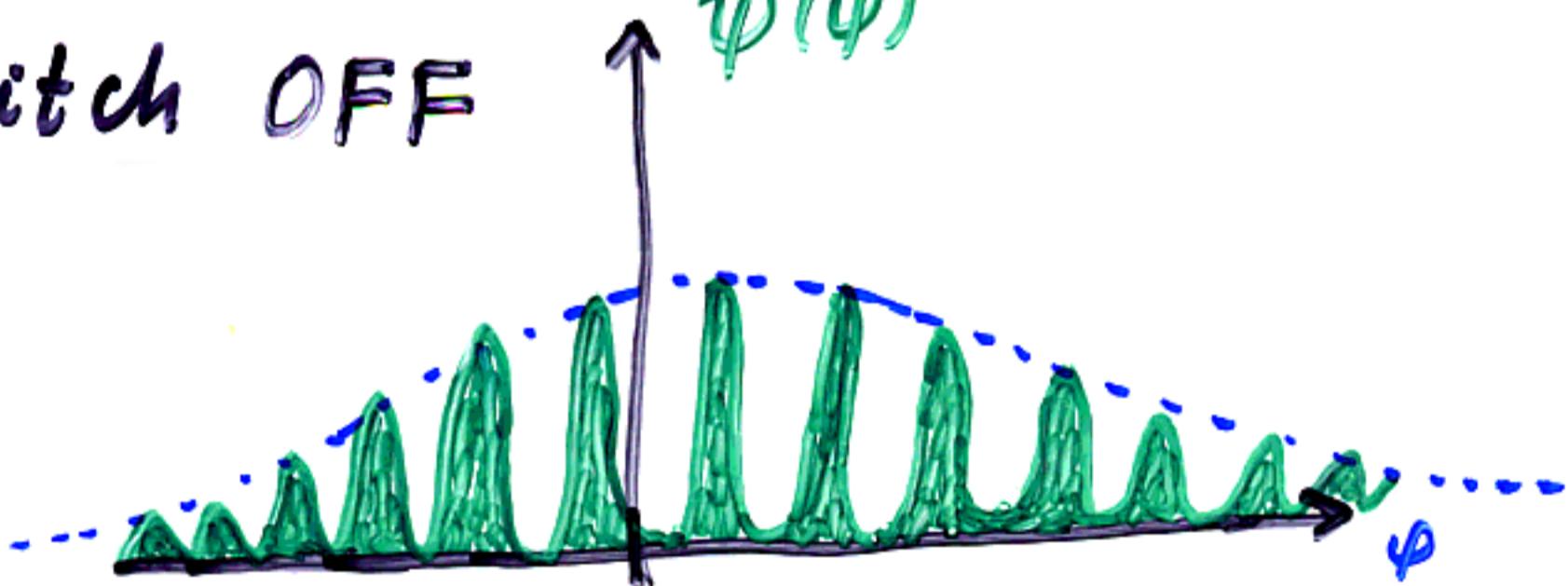

switch ON

$\psi(\varphi)$



The physics is very simple:




$$\psi \approx \theta + 2\pi n$$

1) If $L \rightarrow \infty$ then

$$H \approx -J \cos(\varphi - \theta) + \frac{1}{2c} \left(\frac{\partial}{i\partial\varphi} - n_g \right)^2$$

φ varies from $-\infty$ to $+\infty$

Band structure:

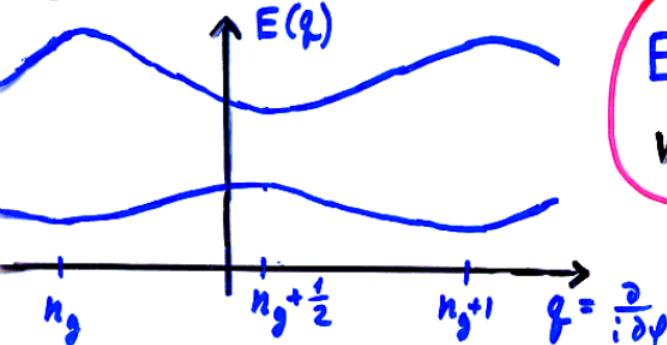

$$E = \frac{1}{c} f(M, q - n_g)$$

where $M = Jc$

2) Reformulating the problem in the charge basis:


$$H_{\text{eff}} = E(q) + \frac{1}{2L} \left(\frac{\partial}{i\partial q} \right)^2$$

If $M = JC \gg 1$ then $E \approx -\frac{t}{C} \cos(2\pi q)$

where $t \sim \mu^{3/4} e^{-8\sqrt{M}}$ ← phase slip amplitude ($\times C$)

Switch is "ON" if $|ct| \ll L^{-1}$
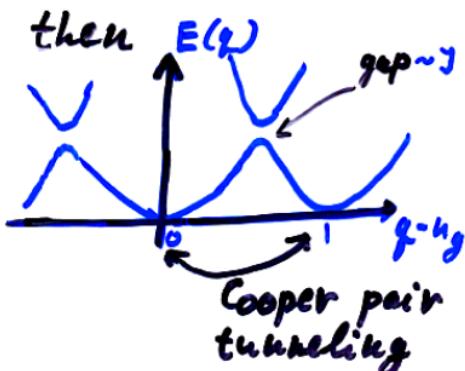
$$\text{If } M = JC \ll 1 \\ E(q) \approx \frac{(q - n_g)^2}{2C}$$




Critical current $I_{\max} \sim$ tunneling amplitude

$$I_{\max} \sim L^{-1} \gamma^{3/2} e^{-\gamma}, \\ \text{where } \gamma = \frac{1}{q} \sqrt{\frac{L}{C}}$$

Caveat : Large numeric factors may be involved.

DC transformer with 1:1 current ratio 11

(current mirror)

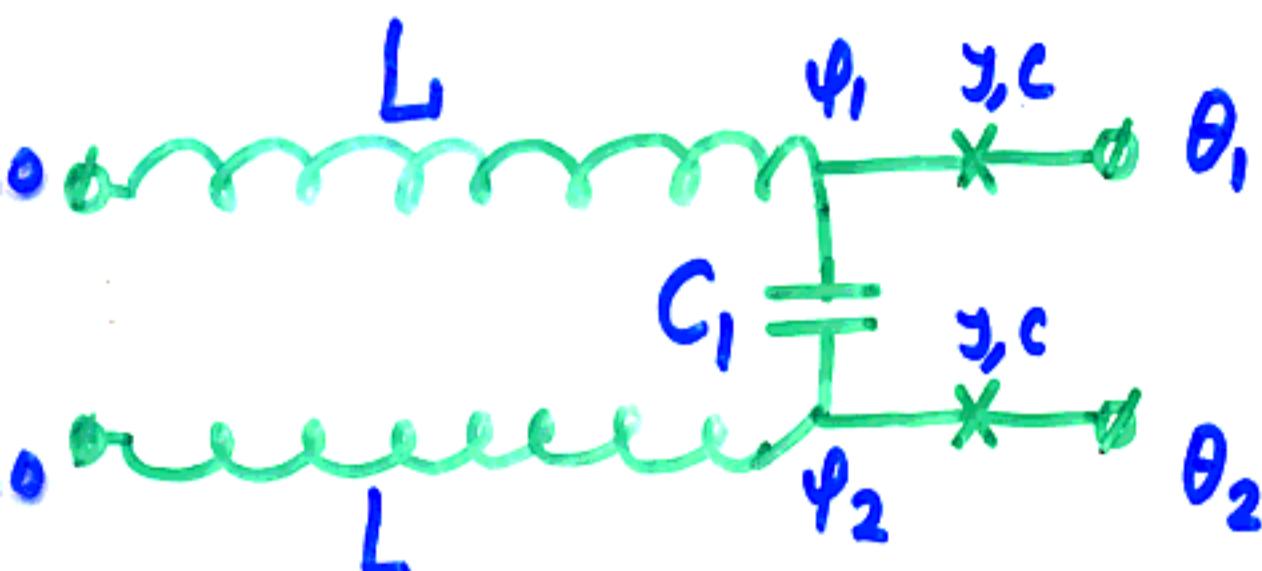

$$4\gamma C \sim 1$$

$$\gamma = \frac{1}{8} \sqrt{\frac{L}{C}} \gg 1$$

$$C_1 \gtrsim C \ln \gamma$$

$$H = \frac{\varphi_+^2}{L} + \frac{\varphi_-^2}{4L} + \frac{q_+^2}{4C} + \frac{q_-^2}{2C_1 + C} - 2\gamma \cos \frac{\varphi_- - \theta_1 + \theta_2}{2} \times \\ \times \cos (\varphi_+ - \theta_1 - \theta_2)$$

where $\varphi_+ = \frac{\varphi_1 + \varphi_2}{2}$, $\varphi_- = \varphi_1 - \varphi_2$

fast

slow

Equivalent circuits :


For φ_+ :



$$I_{max} \sim L^{-1} \gamma e^{-\gamma}$$

(very small)

For φ_- :

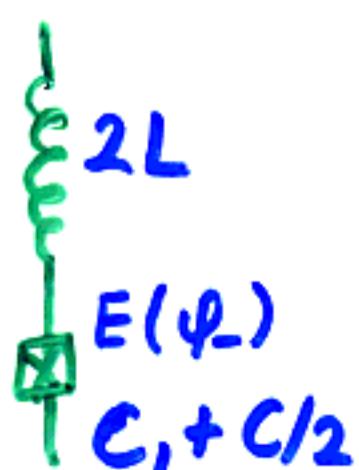


$$I_{max} \sim L^{-1}$$

(sufficiently large)

$$E(\theta_1, \theta_2) = \underbrace{F(\theta_1 - \theta_2)}_{\sim L^{-1} \gamma e^{-r}} + \underbrace{g(\theta_1, \theta_2)}_{\sim L^{-1} \gamma e^{-r}}$$

$$\min_n \frac{1}{4L} (\theta_1 - \theta_2 - 2\pi n)^2$$

More general situation:

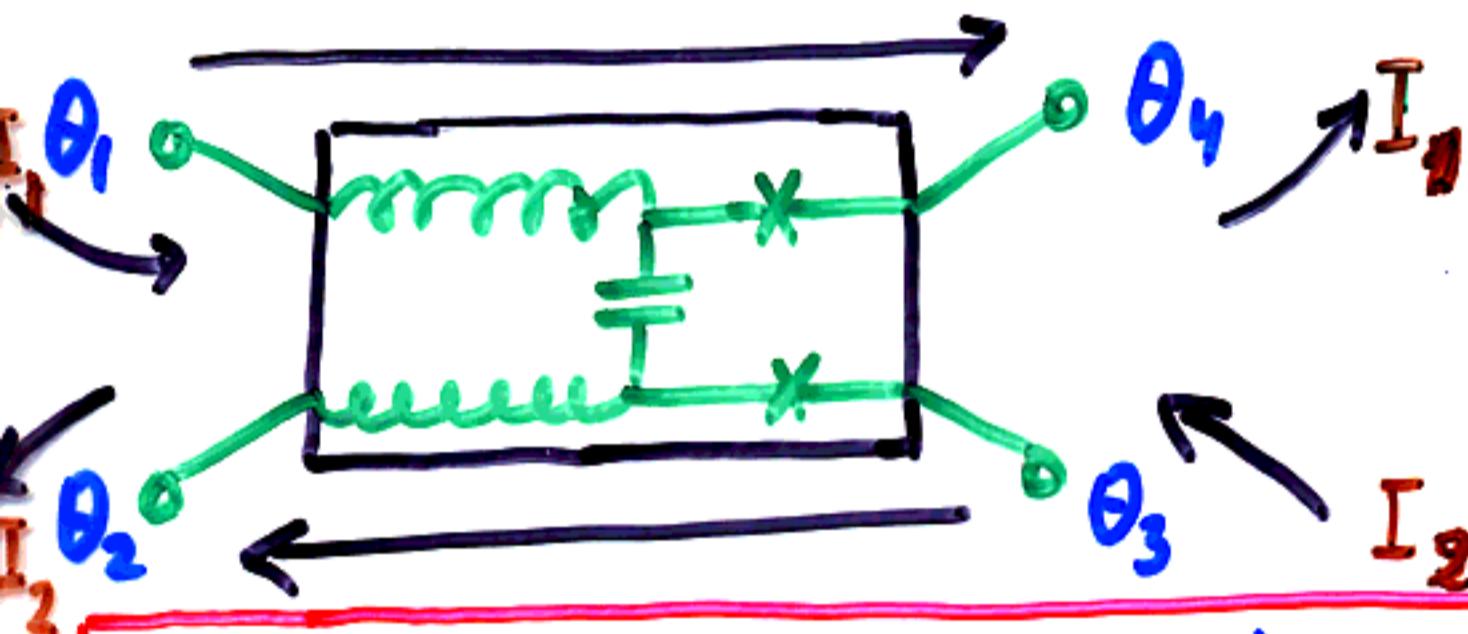


$$E = F(\theta_1 - \theta_2 + \theta_3 - \theta_4) + g(\theta_1, \theta_2, \theta_3, \theta_4)$$

$$I_1 \approx I_2 : \left\{ \begin{array}{l} I_1 - I_2 = \frac{\partial q}{\partial \theta_1} + \frac{\partial q}{\partial \theta_2} \sim L^{-1} \gamma e^{-r} \\ I_1 \approx I_2 < I_{\max} \approx \frac{\pi}{2L} \end{array} \right.$$

$$\text{No dissipation} \Rightarrow V_{14} \approx V_{23}$$

Turning a current mirror into a qubit

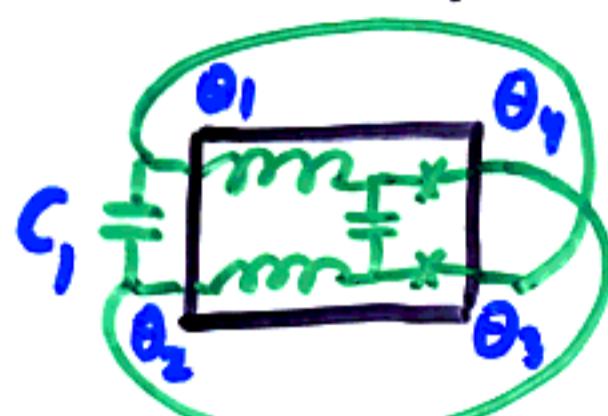


$$\theta_1 = \theta_3$$

$$\theta_2 = \theta_4$$

$$E = F(2(\theta_1 - \theta_2)) + h(\theta_1 - \theta_2)$$

exponentially suppressed

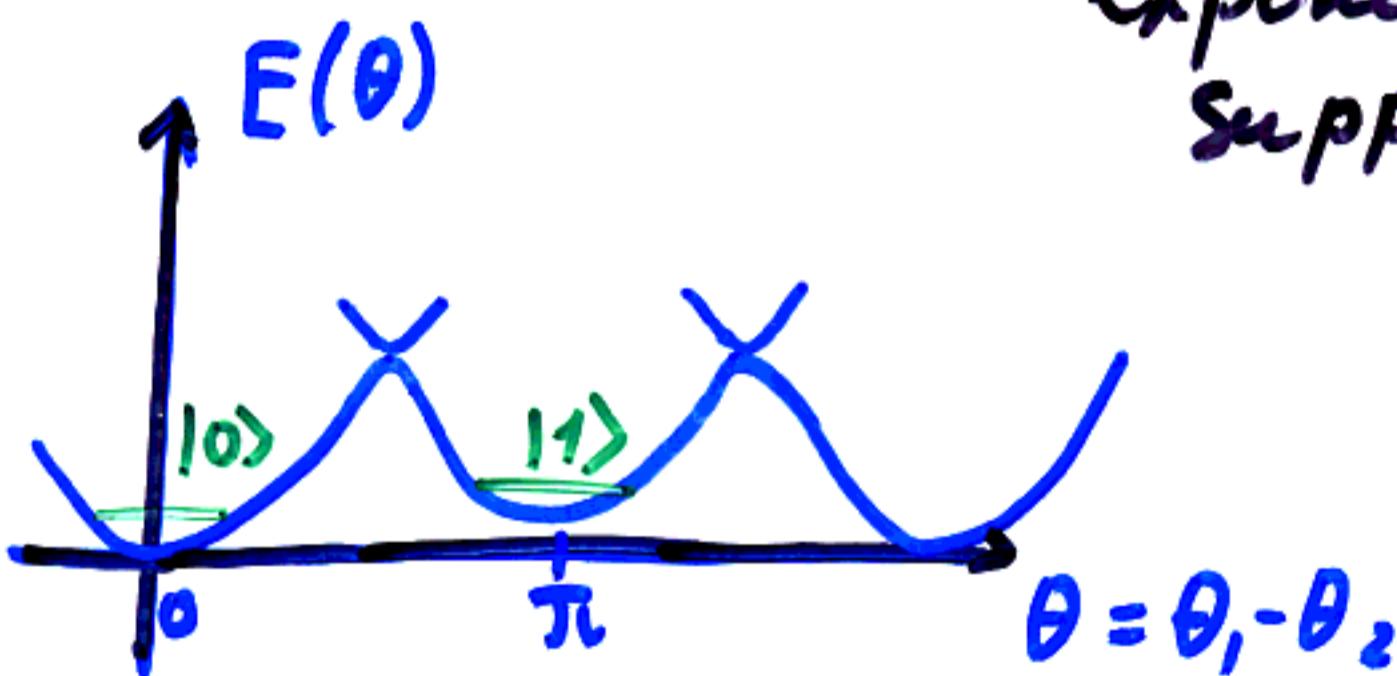

To prevent tunneling $|0\rangle \leftrightarrow |1\rangle$,


we need

$$|JC_1| \gg 1$$

No phase slips in the inductors

Complete qubit

L14

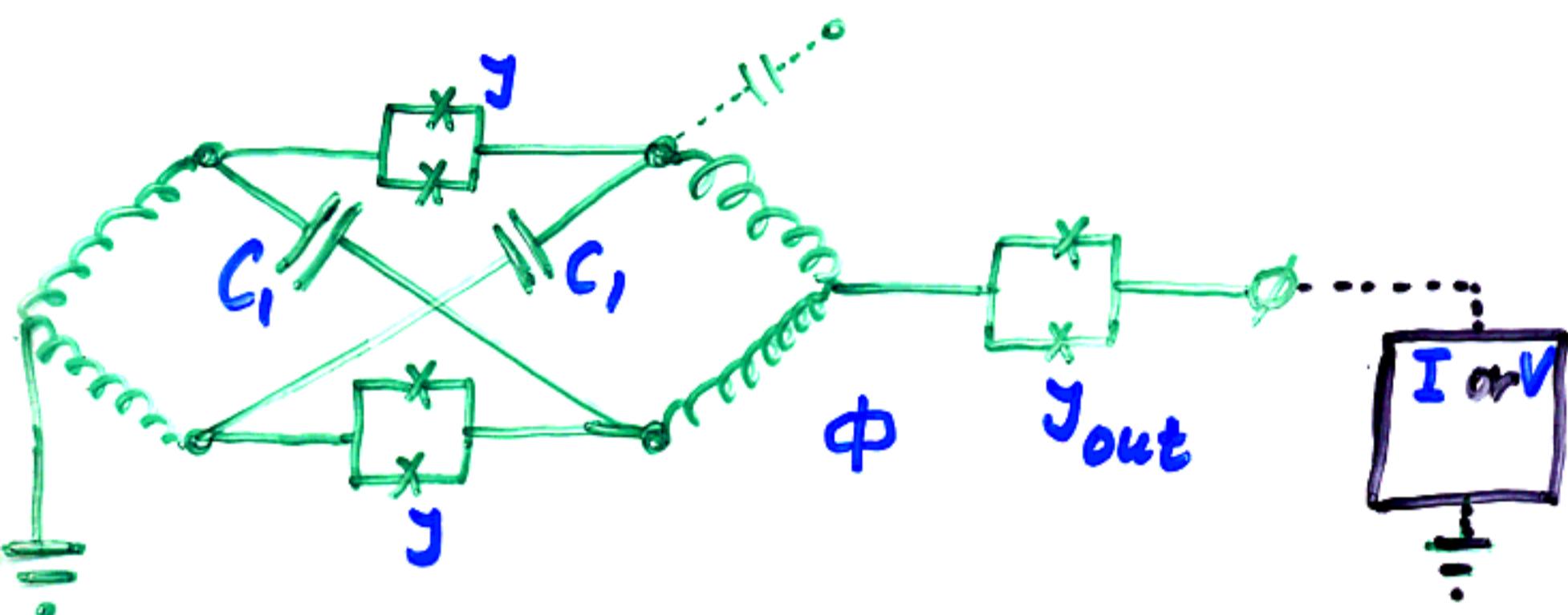

1) Quiet state :

J ON

J_{out} OFF

2) Phase measurement : J ON

$|0\rangle$ vs $|1\rangle$

J_{out} ON

$$I_{\text{out}} \sim \frac{1}{L}$$

3) Dual measurement

$$\frac{|0\rangle + |1\rangle}{\sqrt{2}} \quad \text{vs} \quad \frac{|0\rangle - |1\rangle}{\sqrt{2}}$$

J OFF

J_{out} OFF

$$V_{\text{out}} \sim \frac{1}{C_1}$$

Quantum gates


Universal set:

- 1) Measurement in the $|0\rangle, |1\rangle$ basis
- 2) Measurement in the $|+\rangle, |-\rangle$ basis $|+\rangle = \frac{|0\rangle + |1\rangle}{\sqrt{2}}$ $|-\rangle = \frac{|0\rangle - |1\rangle}{2}$
- 3) $\exp(i\frac{\pi}{4}\sigma^z)$, $\exp(i\frac{\pi}{4}\sigma_z^x\sigma_z^y)$
with high precision (protected)
- 4) $\exp(i\frac{\pi}{8}\sigma^z)$ with low ($\sim 30\%$)
precision (unprotected)

Implementation of the measurements.

|0>, |1>

Measuring the
phase difference
(0 or π)

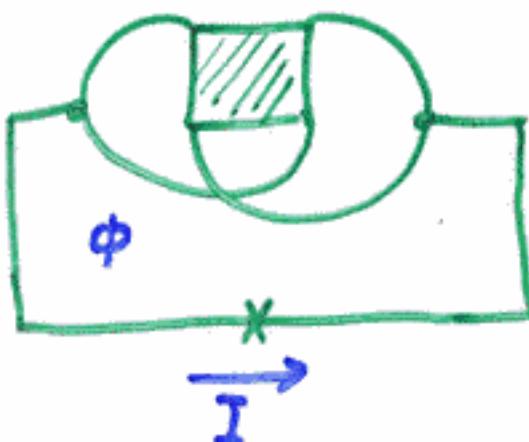

|+> |-> - more interesting

Consider
this setup:



$$H = \frac{1}{2C_{\text{eff}}} (n - n_0 - \hat{\alpha})^2$$

$$\hat{\alpha} = \frac{1 + G^x}{4}$$

$$n = \frac{\partial}{\partial \phi}$$

$$|+\rangle \Rightarrow \underline{\alpha = 0}$$

$$|-\rangle \Rightarrow \underline{\alpha = \frac{1}{2}}$$

Unprotected $\exp(i \frac{\pi}{8} G^z)$:



Connect for time interval Δt

$$|\psi\rangle \mapsto \exp(i \gamma \Delta t G^z) |\psi\rangle$$

Protected $\exp(-i \frac{\pi}{4} G^z)$


Cf. Gottesman
Kitaev, Preskill
2000



Effective circuit:

Connect for
 $\Delta t = \frac{L}{\pi}$

$$|\psi\rangle \mapsto \exp(-i \frac{\phi^2}{2L} \Delta t) |\psi\rangle$$

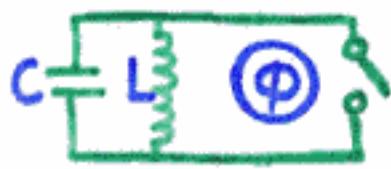

$$\phi = 0 \quad (|0\rangle)$$

or


$$\phi = \pi \quad (|1\rangle)$$

$$|\psi\rangle \mapsto |\psi\rangle$$

$$|\psi\rangle \mapsto -i |\psi\rangle$$

$$R = \sqrt{\frac{L}{C}} \gg 1$$


Actually need
switch:

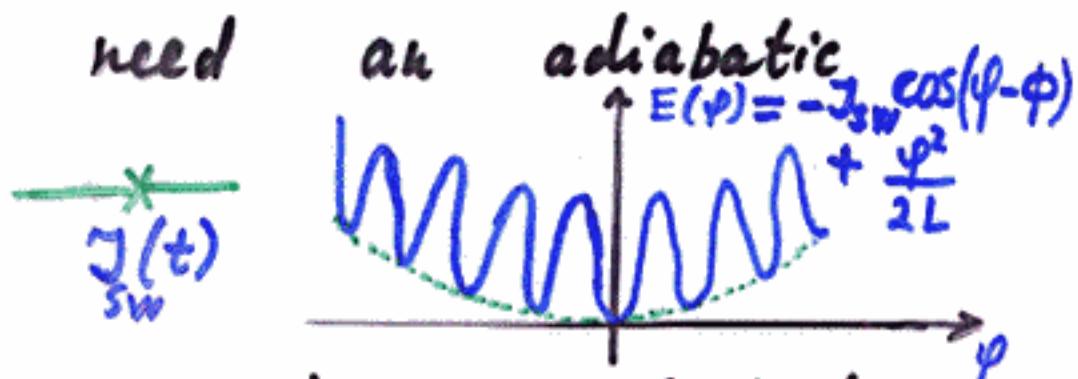

$J_{SW} \lesssim \frac{1}{c}$ — phase is unlocked




$J_{SW} \gg \frac{1}{c}$ — phase is locked

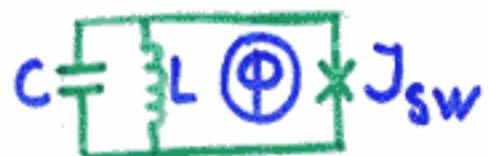
Transition time: $C \ll \tau \ll 2\pi\sqrt{LC}$



not to create
oscillations
in the $J_{SW}-C$
circuit

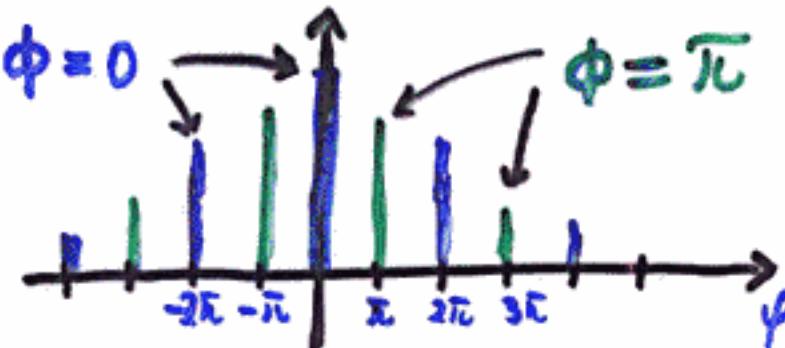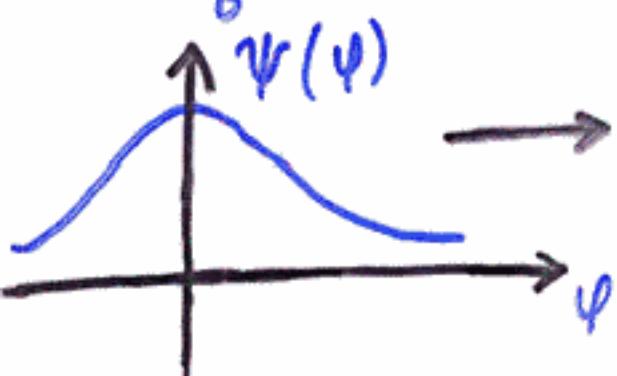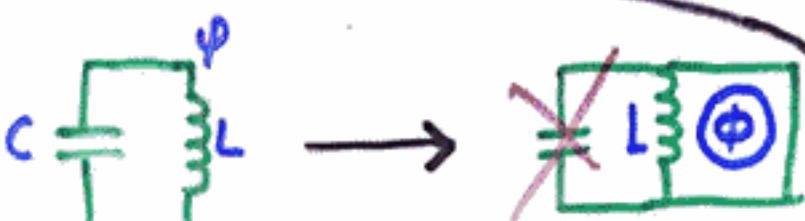to freeze
the zero
oscillations
in the $L-C$
circuit



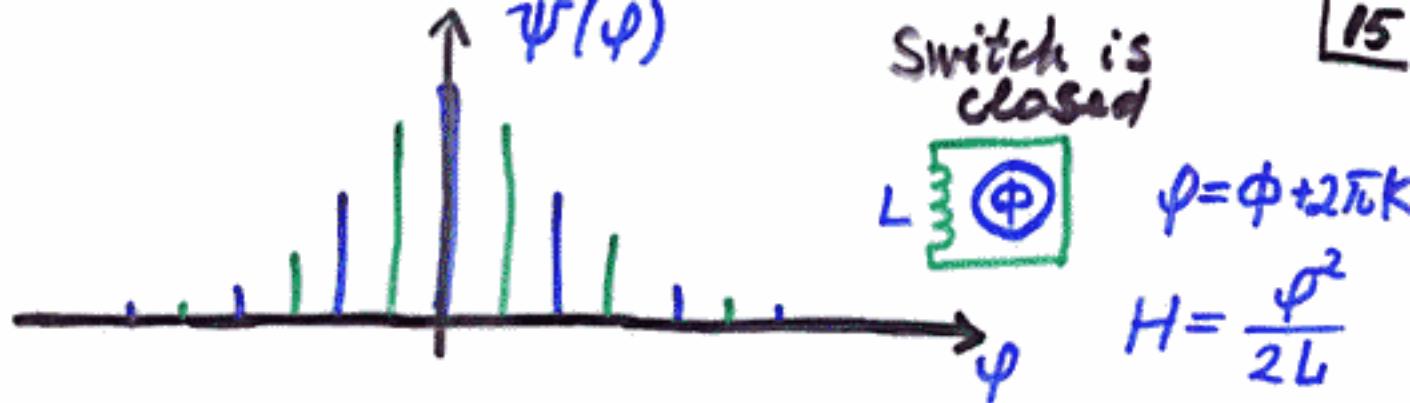

Each blue peak is multiplied by $\exp\left(-i\underbrace{\frac{(2\pi)^2}{L}\Delta t}_{2\pi} K^2\right) = 1$
 ↑ peak #

Each green peak is multiplied by $\exp\left(-i\underbrace{\frac{(2\pi)^2}{L}\Delta t}_{2\pi} (K+\frac{1}{2})^2\right) = -i$

If Δt is not exact, then excitations will be created in the L-C circuit, $C \parallel L$, but the qubit will remain (almost) undisturbed.

Conclusions

- 1) An all-electric QC is possible theoretically
- 2) A lot of fun for theorists; experimental prospects are not clear yet
- 3) In short term (mid term), it would be great to implement a quantum transformer as an analog device.